

TITLE - Verifications of Basic and Universal Gate integrated Circuits

OBJECTIVE - To verify the outputs of all Logic Gates along with their truth tables.

LIST OF APPARATUS - Digital Trainer Kit, wires, Integrated Circuits

We get two kinds of Logic Gates -

- | | |
|--------------------|---------------------|
| • Basic Gates | • Universal Gates |
| → 4071 2-input OR | → 4001 2-input NOR |
| → 4081 2-input AND | → 4011 2-input NAND |
| → 4069 1-input NOT | |
| → 4070 2-input XOR | |

THEORY - The manipulation of binary information is done by logic circuits called "gates". Gates are blocks of hardware that produce signals of 1 and 0 when the input logic requirements are met. This input output relationship of the binary variables for each gate can be represented in a tabular format which is referred as a "truth table". These gates/logic gates can be classified into two types, based on their usage.

- 1) Basic Gates
- 2) Universal Gates

Now, these gates are also sub-divided. There are 4 kinds of Basic gates and 2 kinds of universal gates. The basic gates are OR, AND, XOR and NOT gate. While the universal gates are NOR and NAND gate.

Figure 1 contains the schematic representation of the classification of logic gates.

LOGIC GATES

 


Fig 1: Schematic representation of the classification of Logic Gates

- OR → The OR gate produces the output 1 if the input A or input B or both inputs are 1; otherwise the output is 0.
- AND → The AND gate produces the output 1 if input A and input B, both equals to 1; otherwise the output is 0.
- NOT → The NOT gate, also known as inverter, produced the output 1 if the single input A equals to 0.
- XOR → The output of the XOR gate is 1 if any input is 1 but excludes the combination when both inputs are 1.
- NOR → The NOR gate, or NOT-OR gate, produces the output 0 if input A or input B or both inputs are 1; otherwise the output is 1.
- NAND → The NAND gate, or NOT-AND gate, produces the output 0 if input A and input B, both equal to 1; otherwise the output is 1.

Figure 2 contains the graphical representation of each of the logic gates.


 


Fig 2: Graphical representation of the logic gates

PIN CONFIGURATIONS - The following diagrams are the pin configurations of the given Integrated circuits:-

IC4071 \rightarrow 2-input OR Gate

 


$A, B \rightarrow$ input

$Q \rightarrow$ output


$0V \rightarrow$ Ground connection

$+V_e \rightarrow +5V$ input


IC 4081 → 2-input AND Gate

 


IC 4069 → 1 input NOT Gate

 


IC 4070 → 2 input-XOR gate

 

IC 4001 \rightarrow 2-input NOR Gate

 


IC 4011 \rightarrow 2-input NAND Gate

 

CIRCUIT DIAGRAM: Circuit diagrams for the verification of each logic gates are as follows

$O \rightarrow$ Output

$A, B \rightarrow$ Inputs

 



$$O = A + B$$




$$O = A \cdot B$$


NOT Gate \rightarrow  $O = \bar{A}$

XOR Gate \rightarrow  $O = A \cdot B' + A' \cdot B = A \oplus B$


NOR Gate \rightarrow  $O = \overline{A+B}$



 NAND Gate \rightarrow  $O = \overline{A \cdot B}$




OR Using NOR Gate \rightarrow

 


$$\begin{aligned} O &= \overline{(\overline{A+B}) + (\overline{A+B})} \\ &= \overline{(\overline{A+B})} \\ &= A+B \end{aligned}$$


AND Using NOR Gate \rightarrow

 


$$O = (A' + B') = A \cdot B$$

 NOT Using NOR GateXOR Using NOR Gate

$$\begin{aligned}
 O &= ((A+B)' + A \cdot B)' \\
 &= (A+B) \cdot (AB)' \\
 &= AB' + A'B
 \end{aligned}$$

 OR Using NAND Gate

$$\begin{aligned}
 O &= (A' \cdot B')' \\
 &= A + B
 \end{aligned}$$

 
AND Using NAND Gate

$$\begin{aligned}
 O &= ((A \cdot B)' \cdot (A \cdot B)')' \\
 &= ((A \cdot B)')' = A \cdot B
 \end{aligned}$$

NOT Using NAND Gate

$$O = (A \cdot A)' = A'$$

XOR Using NAND Gate

 

$$O = ((A \cdot (A \cdot B)')') \cdot (B \cdot (A \cdot B)')')'$$

$$= AB' + A'B$$

TRUTH TABLES

OR Gate		
A	B	$O = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

AND Gate		
A	B	$O = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

NOT Gate	
A	$O = A'$
0	1
1	0

XOR Gate		
A	B	$O = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

NOR Gate

A	B	$Q = A + B$	$O = (A + B)'$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

NAND Gate

A	B	$Q = A \cdot B$	$O = (A \cdot B)'$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

OR Using NOR Gate \rightarrow

A	B	$A + B$	$(A + B)'$	$O = ((A + B)' + (A + B)')'$
0	0	0	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	0	1

AND Using NOR Gate-

A	B	$A + A$	$B + B$	A'	B'	$(A' + B)'$	$(A' + B')'$	$O = AB$
0	0	0	0	1	1	1	0	0
0	1	0	1	1	0	1	0	0
1	0	1	0	0	1	1	0	0
1	1	1	1	0	0	0	1	1

NOT Using NOR Gate:

A	$A + A$	$O = (A + A)' = A'$
0	0	1
1	1	0

XOR Using NOR Gate:

A	B	$(A+B)'$	A'	B'	$(A'+B')' = A \cdot B$	$O = ((A+B)' + A \cdot B)'$
0	0	1	1	1	0	0
0	1	0	1	0	0	1
1	0	0	0	1	0	1
1	1	0	0	0	1	0

~~NOR Using NOR Gate:~~

OR Using NAND Gate:

A	B	$(A \cdot A)' = A'$	$(B \cdot B)' = B'$	$O = (A' \cdot B')' = A + B$
0	0	1	1	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	1

AND Using NAND Gate:

A	B	$(A \cdot B)'$	$O = ((A \cdot B)' \cdot (A \cdot B)')' = A \cdot B$
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

NOT using NAND Gate:

A	A-A	$O = (A-A)'$
0	0	1
1	1	0

XOR using NAND Gate:

A	B	$(A \cdot B)'$	$(A \cdot (A \cdot B)')'$	$(B \cdot (A \cdot B)')'$	$O = ((A \cdot (A \cdot B)')' \cdot (B \cdot (A \cdot B)')')'$ $= A\bar{B} + \bar{A}B = A \oplus B$
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	1	1	0

CONCLUSION: In the lab, I explored the function of the basic logic gates. I learned how to implement them on a breadboard with integrated circuits. I tested the output voltage of the circuits and ensured the result corresponded with the truth table of the logic gate tested.