


## Experiment No. 2a

Aim: - Implementation of half adder using logic gates.

Theory: A combinational logic circuit that performs the addition of two data bits A and B called a half adder. Addition will result in two output bits one of which is Sum (S) and the other is Carry bit (C). The Boolean functions describing the half adder are:


$$S = A'B + AB' = A \oplus B$$

$$C = A \cdot B$$

 

Apparatus Required: IC 4081, IC 4070, digital trainer kit

Half Adder Using Basic Gates:

 

TRUTH TABLE:

| INPUT |   | OUTPUT |   |
|-------|---|--------|---|
| A     | B | S      | C |
| 0     | 0 | 0      | 0 |
| 0     | 1 | 1      | 0 |
| 1     | 0 | 1      | 0 |
| 1     | 1 | 0      | 1 |

Half Adder K-map:

For Sum (S):  $S = A \oplus B$

| A \ B | 0 | 1 |
|-------|---|---|
| 0     | 0 | 1 |
| 1     | 1 | 0 |

For Carry (C):  $C = A \cdot B$

| A \ B | 0 | 1 |
|-------|---|---|
| 0     | 0 | 0 |
| 1     | 0 | 1 |

Result: Half adder is constructed and truth table is verified.

## Experiment No: (2b)


Aim: Implementation of Full Adder using logic gates.

Theory: The half adder does not take the carry bit from its previous stage into account. This carry bits from its previous stage is called carry-in bit. A full adder adds three one bit binary numbers - two operands and a carry bit. The adder outputs two numbers, a sum and a carry bit. The boolean functions for describing full adder are:

$$S = A \oplus B \oplus C$$

$$C_{out} = A \cdot B + B \cdot C_{in} + A \cdot C_{in}$$

Full Adder using Basic Gates:

 

Truth Table:

| Input |   |                 | Output |                  |
|-------|---|-----------------|--------|------------------|
| A     | B | C <sub>in</sub> | S      | C <sub>out</sub> |
| 0     | 0 | 0               | 0      | 0                |
| 0     | 0 | 1               | 1      | 0                |
| 0     | 1 | 0               | 1      | 0                |
| 0     | 1 | 1               | 0      | 1                |
| 1     | 0 | 0               | 1      | 0                |
| 1     | 0 | 1               | 0      | 1                |
| 1     | 1 | 0               | 0      | 1                |
| 1     | 1 | 1               | 1      | 1                |
|       |   |                 |        |                  |

K-map for Full Adder:For  $S = A \oplus B \oplus C$ 

| A \ BC | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      | 0  | 1  | 0  | 1  |
| 1      | 1  | 0  | 1  | 0  |

For  $C_{out} = A \cdot B + B \cdot C_{in} + C_{in} \cdot A$ 

| A \ BC | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      | 0  | 0  | 1  | 0  |
| 1      | 0  | 1  | 1  | 1  |

Result:

Full Adder is constructed and its truth table is verified.


Experiment No. 2c

Aim: Implementation of a full adder using two half adders and an OR Gate.

Apparatus Required: IC 4081, IC 4070, IC 4071, Digital trainer kit, wires

Theory: A full adder is a digital circuit that performs addition. A full adder can be constructed from two half adders by connecting A and B input of one half adder, connecting the sum from that to an input to the second adder, connecting the carry in  $C_{in}$  to the other input and OR-ing the two half adders carry outputs to give the final carry output.

Circuit Diagram:

 

Truth table:

| A | B | $C_{in}$ | S | $C_{out}$ |
|---|---|----------|---|-----------|
| 0 | 0 | 0        | 0 | 0         |
| 0 | 0 | 1        | 1 | 0         |
| 0 | 1 | 0        | 1 | 0         |
| 0 | 1 | 1        | 0 | 1         |
| 1 | 0 | 0        | 1 | 0         |
| 1 | 0 | 1        | 0 | 1         |
| 1 | 1 | 0        | 0 | 1         |
| 1 | 1 | 1        | 1 | 1         |

Result:

Full adder using two half adders and OR gate is constructed and its truth table is verified.


## Experiment No. 2d

Aim: Implementation of half subtractor using logic gates

Theory: Subtracting a single bit binary value B from another A produces a difference bit D and a borrow bit  $B_{out}$ . The operation is called half subtraction and the circuit to realize it is called half subtractor. The Boolean functions describing the half subtractor are:

$$D = A \oplus B$$


$$B_{out} = \bar{A} \cdot B$$

 

Apparatus Required:

IC 4070, IC 4069, IC 4081, Digital Trainer's kit, wires.

Circuit Diagram:

 

Truth Table:

| A | B | D | $B_{out}$ |
|---|---|---|-----------|
| 0 | 0 | 0 | 0         |
| 0 | 1 | 1 | 1         |
| 1 | 0 | 1 | 0         |
| 1 | 1 | 0 | 0         |

K-map:

Difference (D):  $D = A \oplus B$

| A \ B | 0 | 1 |
|-------|---|---|
| 0     | 0 | 1 |
| 1     | 1 | 0 |

For Borrow ( $B_o$ ):  $B_{out} = \bar{A} \cdot B$

| A \ B | 0 | 1 |
|-------|---|---|
| 0     | 0 | 1 |
| 1     | 0 | 0 |

Result: Half Subtractor is constructed and truth table is verified.




Aim: Implementation of Full subtractor using logic gates.

Theory: Subtracting two binary values (single bit), B and  $B_{in}$  from a single bit value A produces a difference bit D and a Bout borrow out bit. This is called full subtractor. The Boolean functions describing the full subtractor are:


$$D = A \oplus B \oplus B_{in}$$
 
$$B_{out} = \bar{A} \cdot B + \bar{A} \cdot B_{in} + B \cdot B_{in}$$



Apparatus Required: IC 4081, IC 4070, IC 4069, IC 4071, Digital Trainer kit, Wires

Circuit Diagrams:

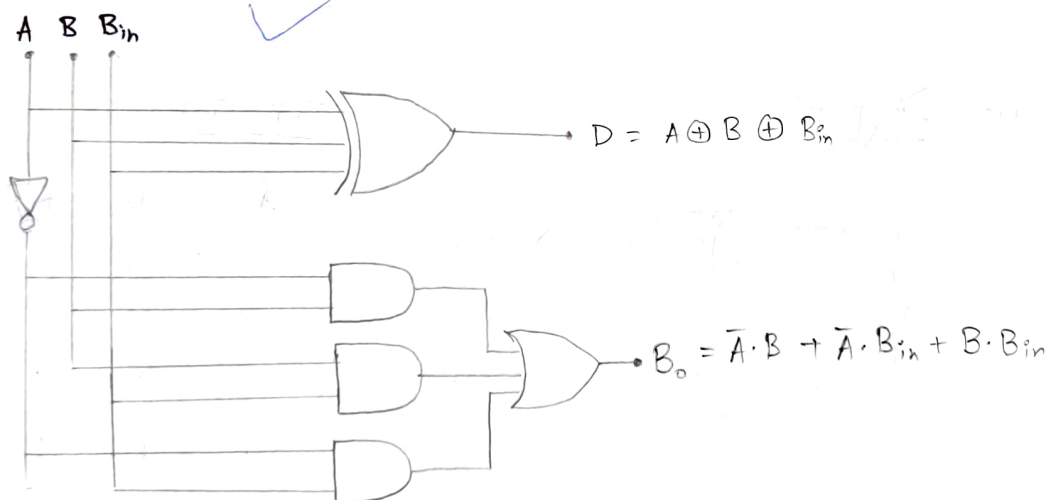

Truth Table:

| INPUT |   |          | OUTPUT |           |
|-------|---|----------|--------|-----------|
| A     | B | $B_{in}$ | D      | $B_{out}$ |
| 0     | 0 | 0        | 0      | 0         |
| 0     | 0 | 1        | 1      | 1         |
| 0     | 1 | 0        | 1      | 1         |
| 0     | 1 | 1        | 0      | 1         |
| 1     | 0 | 0        | 1      | 0         |
| 1     | 0 | 1        | 0      | 0         |
| 1     | 1 | 0        | 0      | 0         |
| 1     | 1 | 1        | 1      | 1         |

K-map:

For Difference

| A \ B B <sub>in</sub> | 00 | 01 | 11 | 10 |
|-----------------------|----|----|----|----|
| 0                     | 0  | 1  | 0  | 1  |
| 1                     | 1  | 0  | 1  | 0  |

$$\begin{aligned}
 D &= A'B'B_{in} + A'BB_{in}' \\
 &\quad + AB'B_{in}' + ABB_{in} \\
 &= A \oplus B \oplus B_{in}
 \end{aligned}$$

For Borrow out

| A \ B B <sub>in</sub> | 00 | 01 | 11 | 10 |
|-----------------------|----|----|----|----|
| 0                     | 0  | 1  | 1  | 1  |
| 1                     | 0  | 0  | 1  | 0  |

$$B_o = A'B_{in} + A'B + BB_{in}$$

Result:

Full subtractor is constructed and truth table is verified


Experiment: 2f

Aim: Implementation of a full subtractor using two half subtractors and OR Gate.

Theory: The full subtractor is a combinational circuit which is used to perform subtraction of three input bits, the minuend, subtrahend, and borrow in. The difference output from the second half subtractor is the XOR of B<sub>in</sub> and the output of the first half subtractor which is same as variance output of full subtractor. This circuit has three inputs and two outputs:

Apparatus Required: IC4081, IC4070, IC4071, IC4069, Digital Trainer kit, wires

### Circuit Diagram:

 

Expression for difference:-

$$\begin{aligned}
 D &= A'B'B_{in} + A'BB_{in}' + AB'B_{in}' + ABB_{in} \\
 &= B_{in}(A'B' + AB) + B_{in}'(AB' + A'B) \\
 &= B_{in}(A \oplus B)' + B_{in}'(A \oplus B) \\
 &= A \oplus B \oplus B_{in}
 \end{aligned}$$

Expression for Borrow Out ( $B_o$ )

$$\begin{aligned}
 B_o &= A'B'B_{in} + A'B \cdot B_{in}' + A'BB_{in} + ABB_{in} \\
 &= A'B'B_{in} + A'BB_{in} + A'BB_{in} + A'BB_{in} + A'BB_{in} \\
 &= A'B_{in}(B+B') + A'B(B_{in} + B_{in}') + BB_{in}(A+A') \\
 &= A'B_{in} + A'B + BB_{in}
 \end{aligned}$$

OR,

$$\begin{aligned}
 B_o &= A'B'B_{in} + A'BB_{in}' + A'BB_{in} + ABB_{in} \\
 &= B_{in}(AB + A'B') + A'B(B_{in} + B_{in}') \\
 &= B_{in}(A \odot B) + A'B
 \end{aligned}$$

Result:

Full subtractor using two subtractors and OR gate is constructed and thus the table is verified.

16 sep 22