

Experiment NO. - 7

Aim: Building a 2bit comparator using logic gates.

Component Required: Digital trainer kit, XOR Gate, OR Gate, AND Gate, NOT Gate and Copper Wires.

Theory: A comparator is a combinational logic circuit which compares 2 binary numbers (N_1 and N_2) and determines if N_1 is lesser than (LT)/ equals to (EQ) / greater than (GT) N_2 .


A 2bit comparator has two input lines for each of the 2-bit binary numbers, with three distinct output lines, which denotes LT, EQ and GT respectively. IF one of three outputs ^{is} ~~is~~ 1, then rest are 0.

Because two numbers can attain only one state from the following -

i) $A < B$, ii) $A = B$, iii) $A > B$. Here Binary numbers are represented as

$N_1 = A_1A_0$ and $N_2 = B_1B_0$ (A_1, A_0 and B_1, B_0 being the bit of the two numbers respectively).

Block Diagram:

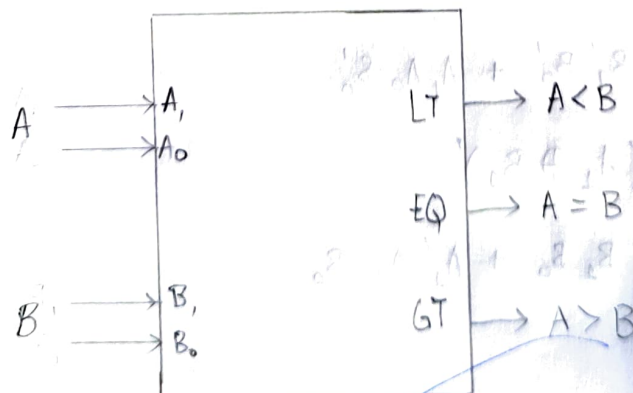

Truth Table:

INPUTS				OUTPUTS		
A_1	A_0	B_1	B_0	$GT(A > B)$	$EQ(A = B)$	$LT(A < B)$
0	0	0	0	0	1	0
		0	1	0	0	1
		1	0	0	0	1
		1	1	0	0	1
0	1	0	0	1	0	0
		0	1	0	1	0
		1	0	0	0	1
		1	1	0	0	1
1	0	0	0	1	0	0
		0	1	1	0	0
		1	0	0	1	0
		1	1	0	0	1
1	1	0	0	1	0	0
		0	1	1	0	0
		1	0	1	0	0
		1	1	0	1	0

Equation for GT, EQ, LT obtained from the truth table are


$$GT - A_1 B_1' + A_0 B_1' B_0' + A_1 A_0 B_0'$$

$$EQ - (A_0 \oplus B_0)' (A_1 \oplus B_1)'$$


$$LT - A_1' B_1 + A_0' B_1 B_0 + A_1' A_0' B_0$$

Circuit Diagrams:


A_1 A_0 B_1 B_0

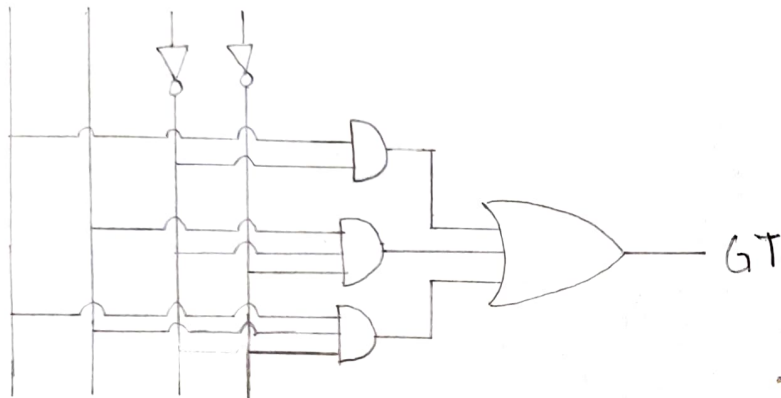

A_1 A_0 B_1 B_0

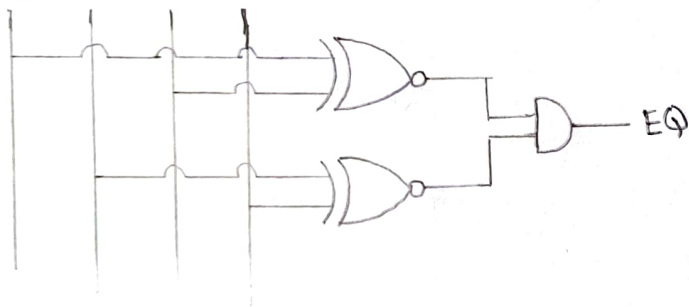

A_1 A_0 B_1 B_0

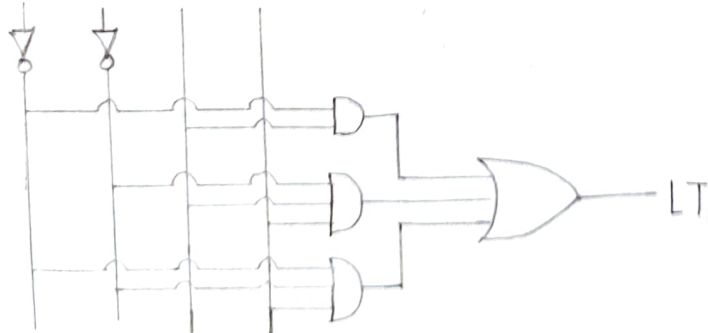

Result: 2 bit comparator circuit was made and its truth table is verified.

Handwritten signature
24/10